

Math 369: Day 9

Application: Electrical Circuits

One place linear algebra turns out to be very useful is in analysis of networks. One example is in electrical circuits, where the key laws are:


Ohm's Law: The voltage drop V due to a current I through a resistor w/ resistance R is

$$V = IR$$

Kirchhoff's Current Law: For any point in the network, the flow in equals the flow out.

Kirchhoff's Voltage Law: Around any closed loop, the net voltage drop is 0.

Ex:

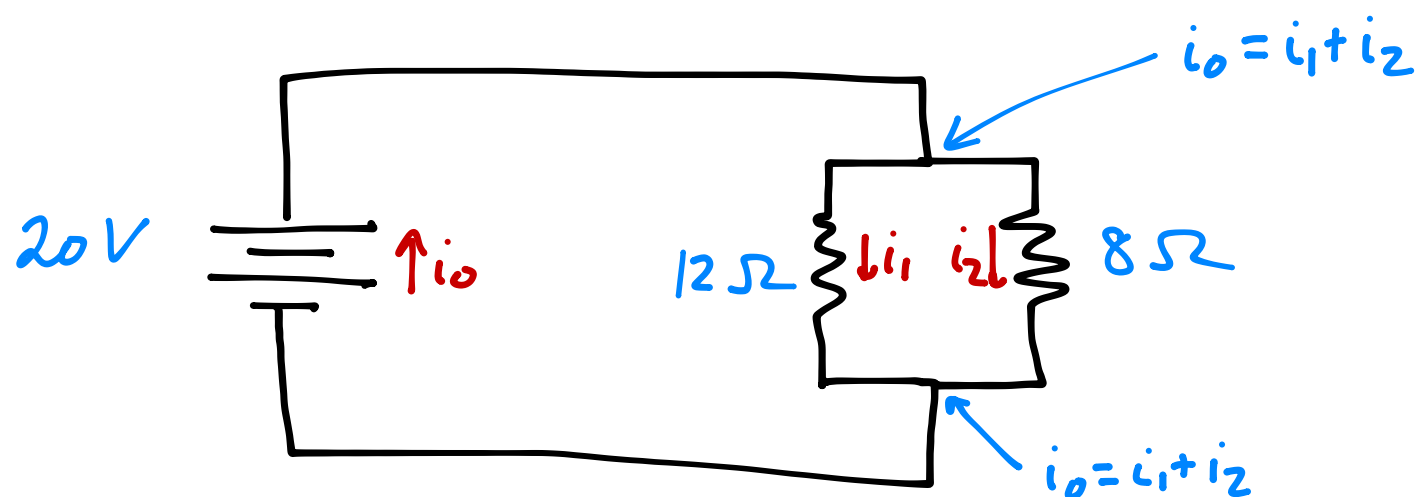

"Inner" loop: $20 - 12i_1 = 0$

"Outer" loop: $20 - 8i_2 = 0$

Small loop: $12i_1 = 8i_2$ or $12i_1 - 8i_2 = 0$


So to determine i_0, i_1, i_2 , need to solve the (redundant) system

$$\begin{aligned} i_0 - i_1 - i_2 &= 0 \\ i_0 - i_1 - i_2 &= 0 \\ 12i_1 &= 20 \\ 8i_2 &= 20 \\ 12i_1 - 8i_2 &= 0 \end{aligned}$$

Obviously, we don't really need any linear system to solve this:

$$\begin{aligned} i_1 &= \frac{20}{12} = \frac{5}{3} \\ i_2 &= \frac{20}{8} = \frac{5}{2} \\ i_0 &= i_1 + i_2 = \frac{25}{6} \end{aligned}$$

Ex: Wheatstone bridge

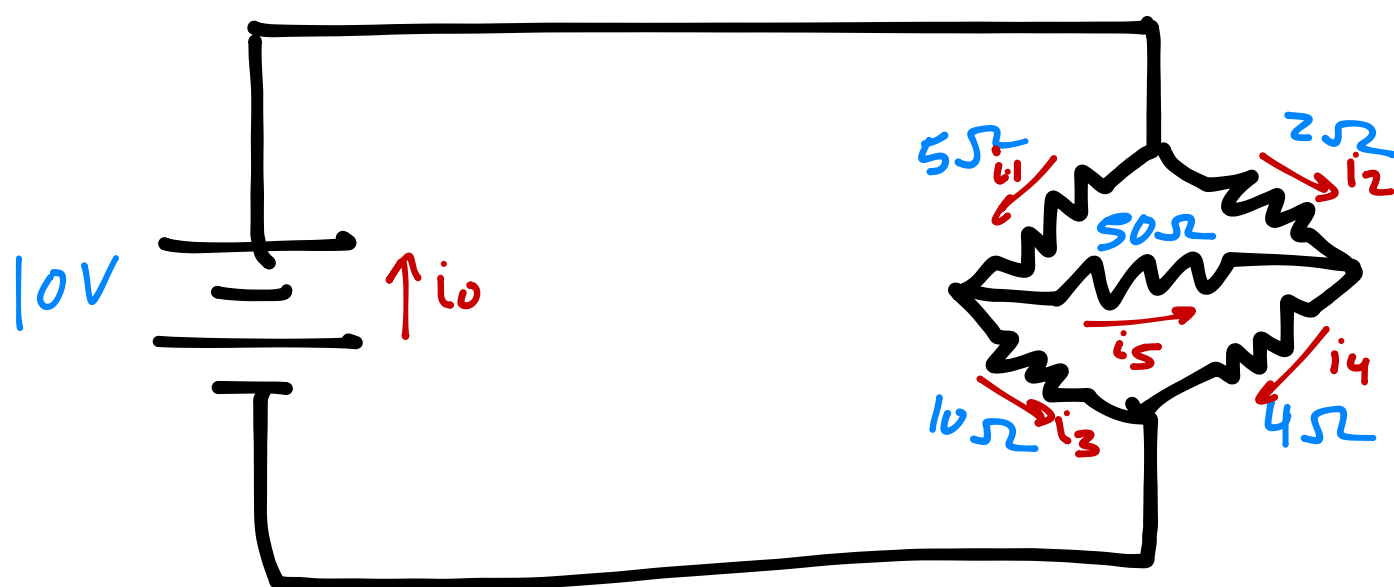


$$\begin{aligned} i_0 &= i_1 + i_2 \\ i_0 &= i_3 + i_4 \\ i_1 &= i_3 + i_5 \\ i_2 + i_5 &= i_4 \\ 5i_1 + 10i_3 &= 10 \\ 2i_1 + 4i_4 &= 10 \\ 5i_1 + 50i_5 - 2i_2 &= 0 \\ 50i_5 + 4i_4 - 10i_3 &= 0 \end{aligned}$$

$$\left[\begin{array}{cccccc|c} 1 & -1 & -1 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & -1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 0 & -1 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 5 & 0 & 10 & 0 & 0 & 10 \\ 0 & 2 & 0 & 0 & 4 & 0 & 10 \\ 0 & 5 & -2 & 0 & 0 & 50 & 0 \\ 0 & 0 & 0 & -10 & 4 & 50 & 0 \end{array} \right]$$

Solution (after some work): $i_0 = 7/3, i_1 = 2/3, i_2 = 5/3, i_3 = 2/3, i_4 = 5/3, i_5 = 0$

Prop: For a general Wheatstone bridge:

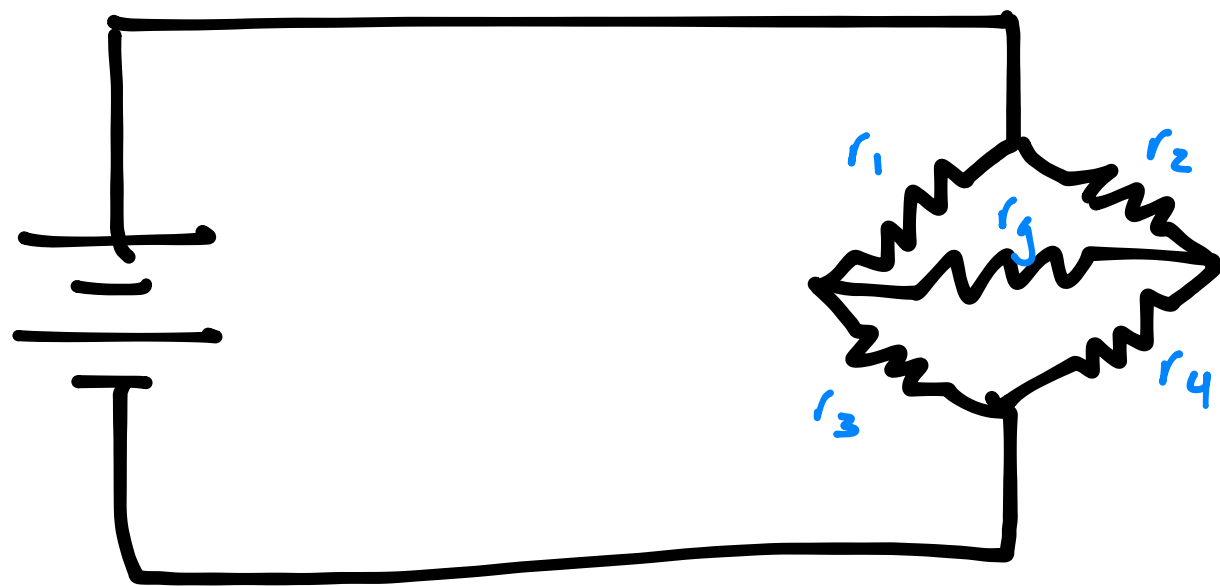

If the current through i_g is 0 then $\frac{r_2}{r_1} = \frac{r_4}{r_3}$

(In practice, one doesn't know r_4 & puts an ammeter at i_g , then adjusts r_1 , r_2 , & r_3 until the current at the meter is 0, then declares $r_4 = \frac{r_2 r_3}{r_1}$)

Pf: Using Kirchhoff's voltage law, $i_1 r_1 + i_g r_g - i_2 r_2 = 0$ & $i_4 r_4 + i_g r_g - i_3 r_3 = 0$

Also, if $i_g = 0$ we get $i_2 r_2 = i_1 r_1 \Leftrightarrow \frac{r_2}{r_1} = \frac{i_1}{i_2}$ & also $i_3 r_3 = i_4 r_4 \Leftrightarrow \frac{r_4}{r_3} = \frac{i_3}{i_4}$.

But now $i_3 = i_1$ & $i_4 = i_2$, so $\frac{r_2}{r_1} = \frac{i_1}{i_2} = \frac{i_3}{i_4} = \frac{r_4}{r_3}$.

QED